
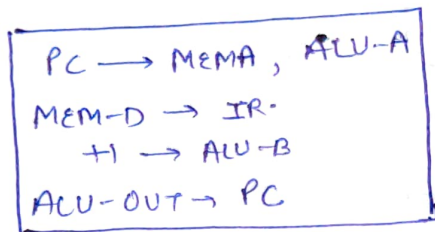



1. ADD RC, RA, RB / 6. NDU RC, RA, RB

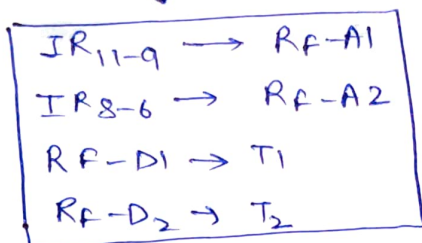


S1



S2.

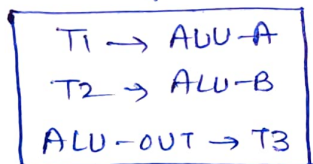


S3

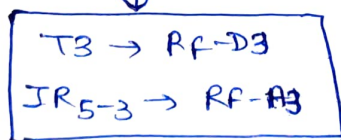


S4

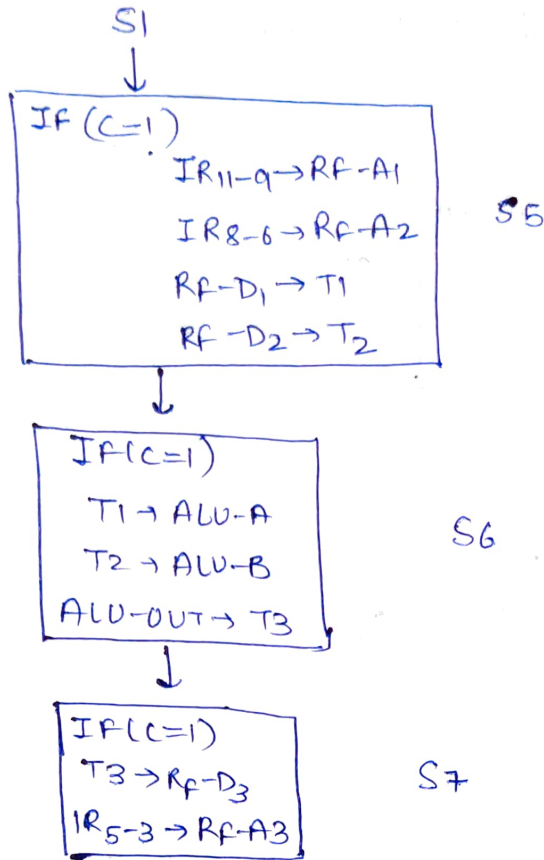2. ADC R_C, R_A, R_B / 7. NDC R_C, R_A, R_B




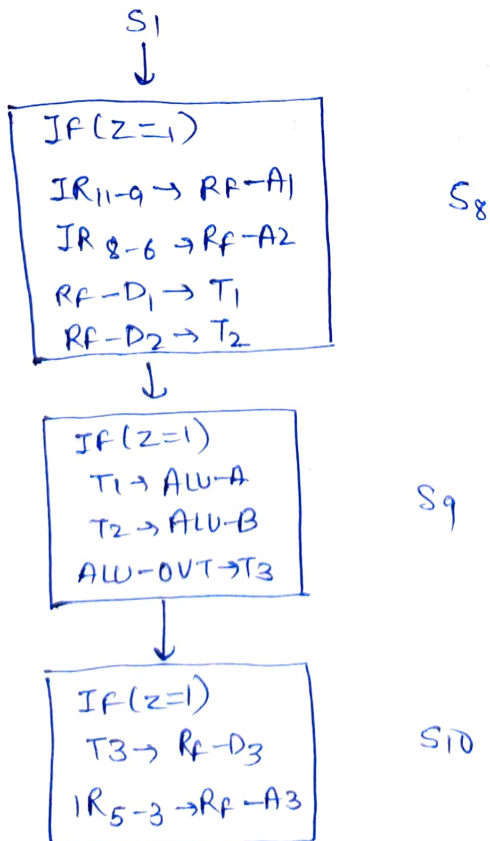3. ADZ R_C, R_A, R_B / 8. NDZ R_C, R_A, R_B




4.

ADD RC, RA, RB

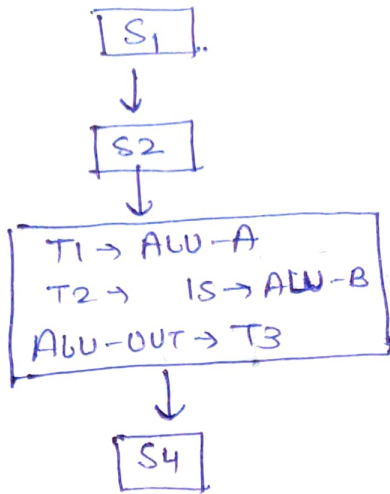

S_{11}

5. ADI RB, RA, IMM6

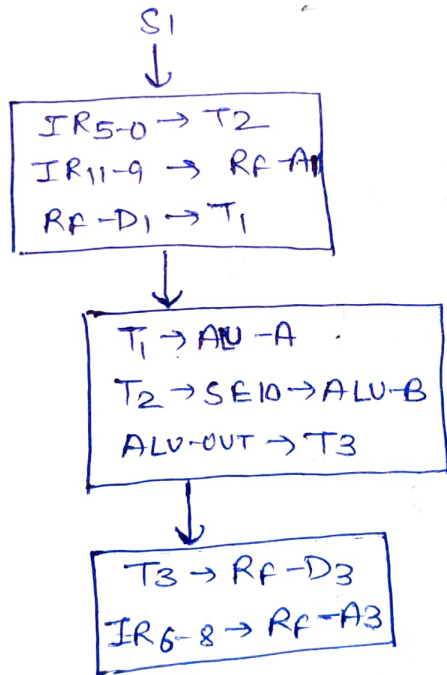


S_{12}


S_{13}

S_{14}


9. LHI RA, IMM

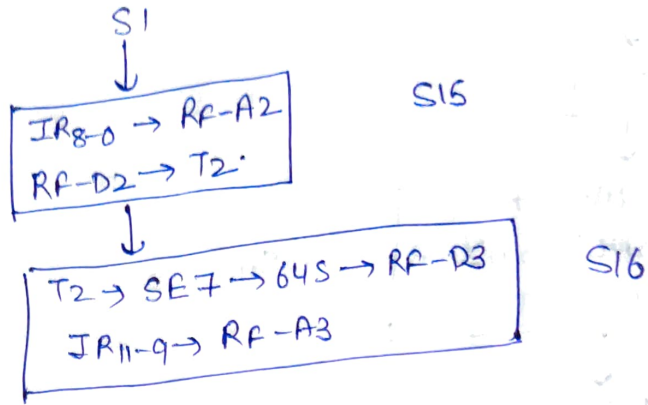


10. LW RA, RB, IMM

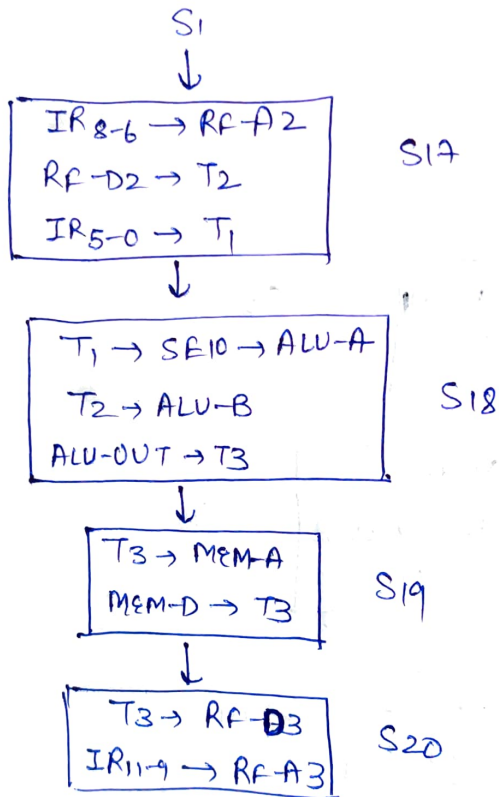

11.

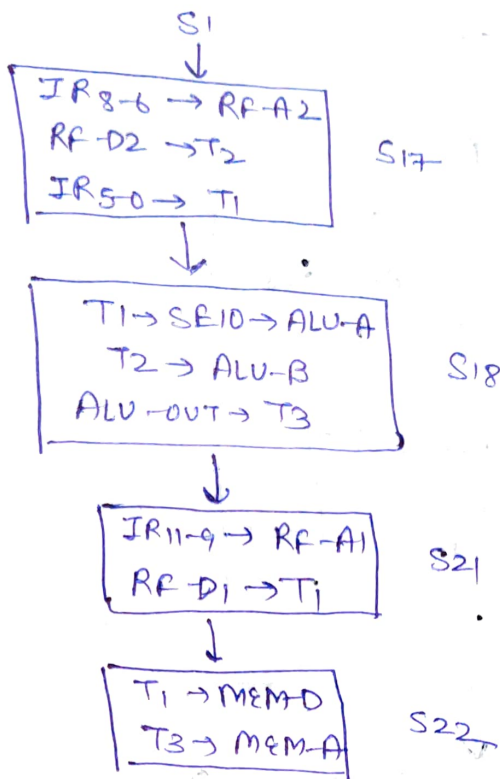
SW RA, RB, IMM

12.

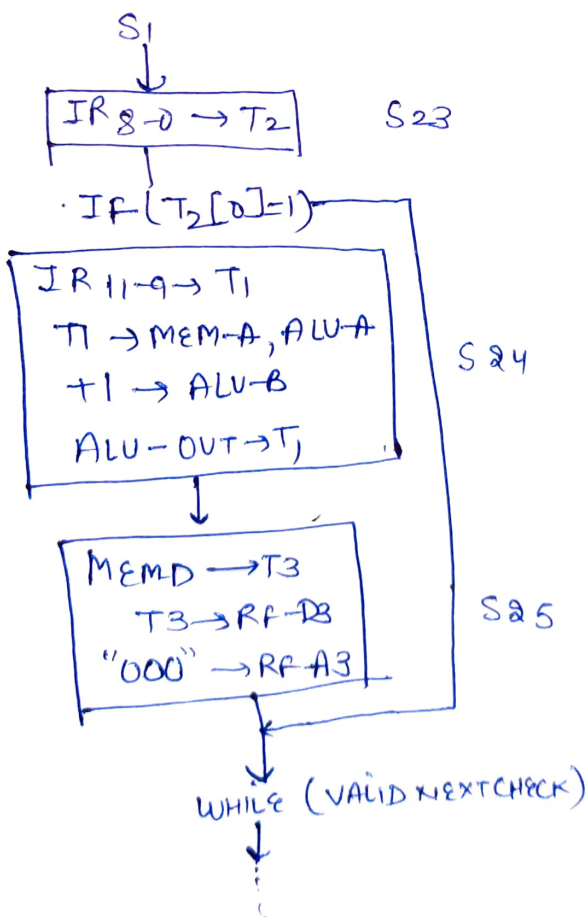LM RA, IMM


13.

SM RA, IMM

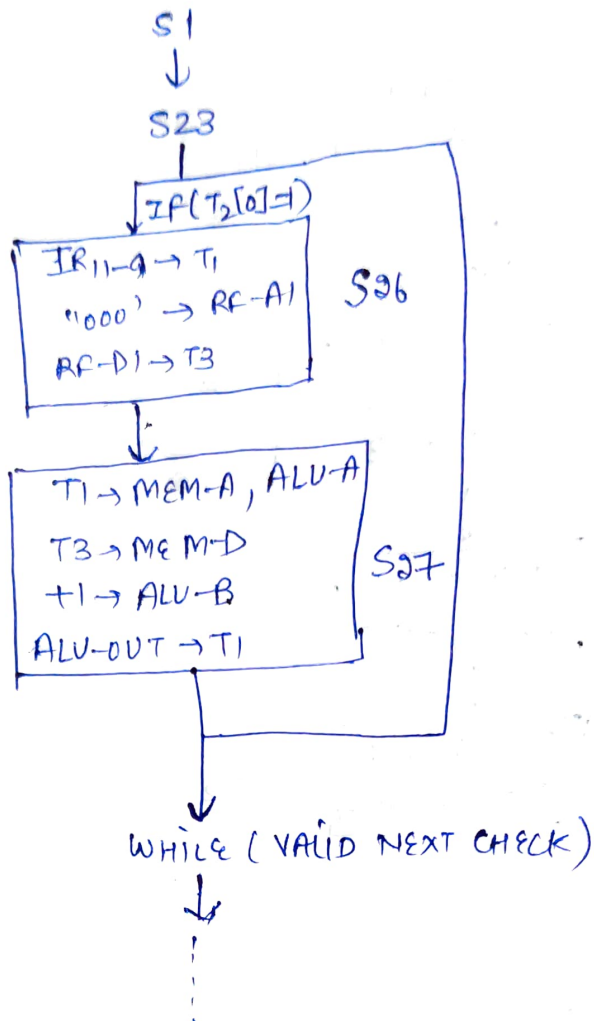


14.

BEO RA, RB, IMM

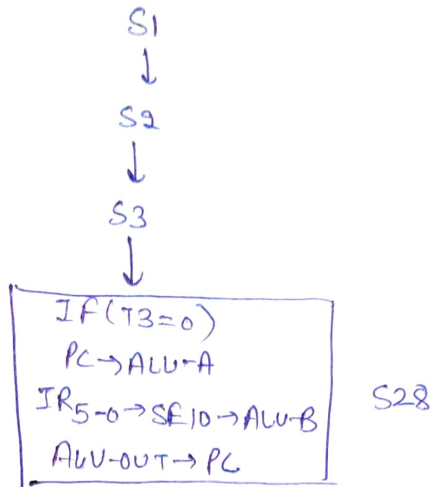


15.

JAL RA, IMM

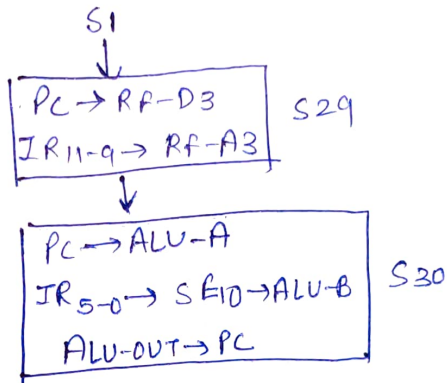


16.

JLR RA, RB

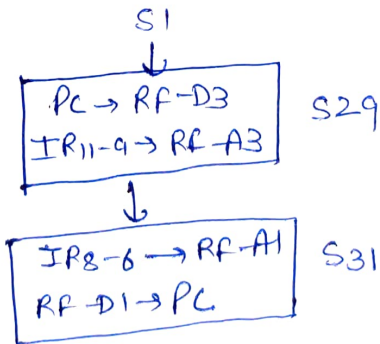

17.

JRI RA, IMM

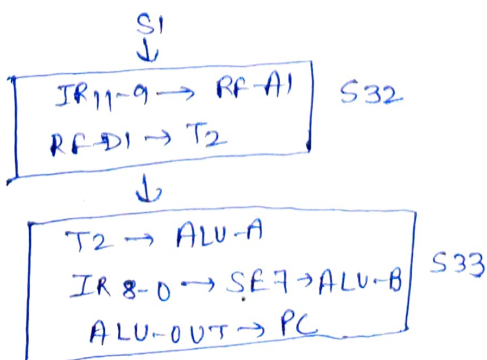

CONTROL STORE

1) ALU

The ALU performs basic operations like add, OR, XOR, AND etc. by taking two inputs ALU-A & ALU-B of 16 bits each. Its output is represented as ALU-out. The instructions are given directly & multiple control lines are used to control the activities inside ALU.

2) TEMPORARY REGISTERS (T₁, T₂, T₃)

Temporary registers store the values for future use. They are all of 16-bits each.

3. MEMORY (MEM)

Memory stores various data at particular locations called addresses. We can access data by providing the address as input (16-bit) through MEM-A & accessing it through MEM-D. We can also store data in memory by providing data to be stored in MEM-D and address in MEM-A.

4. SE7, SE10 (SIGN EXTENDER)

The sign extender places the corresponding number of zeros (7810 resp) to the left of input so as to make it a 16-bit input.

5. LS & RS

This is basically used to shift the input by n bits to the left (127 resp). The digits which are pushed off are eliminated & zeros are added to the right.

6. REGISTER FILE (RF)

It includes all the registers (R_0 to R_7). It has 3 address selection lines (A_1, A_2, A_3) and 3 data output lines D_1, D_2 & D_3 .

To access a value inside register, we have to pass the address of that register in one of the two address lines A_1 & A_2 . and the corresponding output is received at D_1 or D_2 .

To store a data in a register the data is sent to the D_3 selection line & the address of the register is sent as input in A_3 .

R_7 register stores the value of Program Counter (PC)

7. INSTRUCTION REGISTER (IR)

IR is a special purpose register, which is used to receive the 16 bits of instruction. There are three different types of Instruction format (R, I & J type) which allot bits differently to various operands. Following is the bit distribution

R-type

$R_C \rightarrow IR_{5-3}$

$R_B \rightarrow IR_{8-6}$

$R_A \rightarrow IR_{11-9}$

I-type

$IMM \rightarrow IR_{0-5}$

$R_B \rightarrow IR_{8-6}$

$R_A \rightarrow IR_{11-9}$

J-type

$IMM \rightarrow IR_{8-0}$

$R_A \rightarrow IR_{11-9}$